

## 实验 2 带控制端的 8 位运算器设计

### 一、实验目的

- (1) 掌握加法器的设计方法。
- (2) 掌握测试文件的设计方法。
- (3) 掌握 FPGA 技术的层次化设计方法。
- (4) 掌握 FPGA 下载测试方法。

### 二、实验主要仪器设备

- (1) FPGA 实验板
- (2) FPGA 实验板配套软件，ModelSim 仿真软件

### 三、设计任务与要求

#### 1. 基本任务及要求

(1) 用 Verilog 设计一个带低有效控制端的一位全加器，再利用级联方法构成带低有效控制端的 8 位加法器。

(2) 用 Verilog 测试文件，实现 ModelSim 时序仿真。

(3) 根据 FPGA 开发板，配置输入和输出管脚，生成下载文件，实现下载测试。

#### 2. 扩展任务及要求

(1) 用 Verilog 设计带低有效控制端的 4 位并行进位加法器，再利用层次设计方法构成带低有效控制端的 8 位并行加法器。

(2) 用 Verilog 设计加减运算器，通过控制端完成 8 位加法和 8 位减法的转换。

(3) 用 Verilog 测试文件，实现 ModelSim 时序仿真。

(4) 根据 FPGA 开发板，配置输入和输出管脚，生成下载文件，实现下载测试。

## 四、实验内容与步骤

### 1. 基本任务

#### (1) 带低有效控制端的 1 位全加器


##### (a) 工作原理

用门电路实现两个二进制数相加并求出和的组合线路，可以处理低位进位，并输出本位加法进位。

##### (b) Verilog 源程序

```
module full_add(  
    input wire Ai,  
    input wire Bi,  
    input wire Ci,  
    input wire E,  
    output reg Si,  
    output reg Ciout  
);  
  
    wire S = Ci ^ Ai ^ Bi;  
    wire C = Ai & Bi | (Ai ^ Bi) & Ci;  
  
    always @ (*) begin  
        if (E == 1'b0) begin  
            Si = S;  
            Ciout = C;  
        end else begin  
            Si = 1'bz;  
            Ciout = 1'bz;  
        end  
    end  
end  
endmodule
```


##### (c) RTL 视图

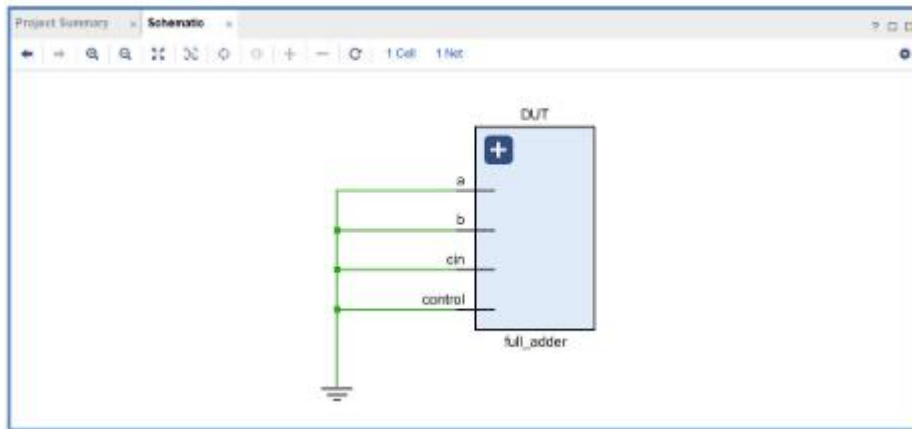

(d) ModelSim 源程序

```
module add_tb();
reg Ain,Bin;
reg clk;
wire sum1,cout1;
initial
begin
    #10
    Ain=0;
    Bin=0;
    clk=0;
end
always #5 clk = ~clk;
always @(posedge clk)
begin
    Ain={$random}%2;
    Bin={$random}%2;
end
add u1(.a(Ain),
.b(Bin),
.sum(sum1),
.cout(cout1));
endmodule
```

(d) ModelSim 仿真结果

 

(e) 下载测试结果

管脚配置

```
set_property -dict {PACKAGE_PIN B24 IOSTANDARD LVCMOS33} [get_ports {Si}]
set_property -dict {PACKAGE_PIN E21 IOSTANDARD LVCMOS33} [get_ports {Ciout}]
set_property -dict {PACKAGE_PIN T3 IOSTANDARD LVCMOS33} [get_ports {Ai}]
set_property -dict {PACKAGE_PIN J3 IOSTANDARD LVCMOS33} [get_ports {Bi}]
set_property -dict {PACKAGE_PIN M2 IOSTANDARD LVCMOS33} [get_ports {Ci}]
set_property -dict {PACKAGE_PIN P1 IOSTANDARD LVCMOS33} [get_ports {E}]
```

(2) 由 1 位全加器级联 8 位加法器

(a) 工作原理

八个一位全加器组级联

(b) Verilog 源程序

```
module full_add(

    input wire Ai,

    input wire Bi,

    input wire Ci,

    input wire E,

    output reg Si,

    output reg Ciout

);

    wire S = Ci ^ Ai ^ Bi;

    wire C = Ai & Bi | (Ai ^ Bi) & Ci;
```

```
always @ (*) begin

    if (E == 1'b0) begin

        Si = S;

        Ciout = C;

    end else begin

        Si = 1'bz;

        Ciout = 1'bz;

    end

end

endmodule
```

```
module add(

    input wire [7:0] A,

    input wire [7:0] B,

    input wire E,

    input wire C0,

    output wire [7:0] S,

    output wire C8

);

    wire C1, C2, C3, C4, C5, C6, C7;
```

```
    full_add f0(
```

```
.Ai(A[0]),  
  
.Bi(B[0]),  
  
.Ci(C0),  
  
.E(E),  
  
.Si(S[0]),  
  
.Ciout(C1)  
  
);
```

```
full_add f1(  
  
.Ai(A[1]),  
  
.Bi(B[1]),  
  
.Ci(C1),  
  
.E(E),  
  
.Si(S[1]),  
  
.Ciout(C2)  
  
);
```

```
full_add f2(  
  
.Ai(A[2]),  
  
.Bi(B[2]),  
  
.Ci(C2),  
  
.E(E),  
  
.Si(S[2]),
```

.Ciout(C3)

);

full\_add f3(

.Ai(A[3]),

.Bi(B[3]),

.Ci(C3),

.E(E),

.Si(S[3]),

.Ciout(C4)

);

full\_add f4(

.Ai(A[4]),

.Bi(B[4]),

.Ci(C4),

.E(E),

.Si(S[4]),

.Ciout(C5)

);

full\_add f5(

.Ai(A[5]),

```
.Bi(B[5]),  
  
.Ci(C5),  
  
.E(E),  
  
.Si(S[5]),  
  
.Ciout(C6)  
  
);
```

```
full_add f6(  
  
.Ai(A[6]),  
  
.Bi(B[6]),  
  
.Ci(C6),  
  
.E(E),  
  
.Si(S[6]),  
  
.Ciout(C7)  
  
);
```


```
full_add f7(  
  
.Ai(A[7]),  
  
.Bi(B[7]),  
  
.Ci(C7),  
  
.E(E),  
  
.Si(S[7]),  
  
.Ciout(C8)
```



);

endmodule

(c) RTL 视图

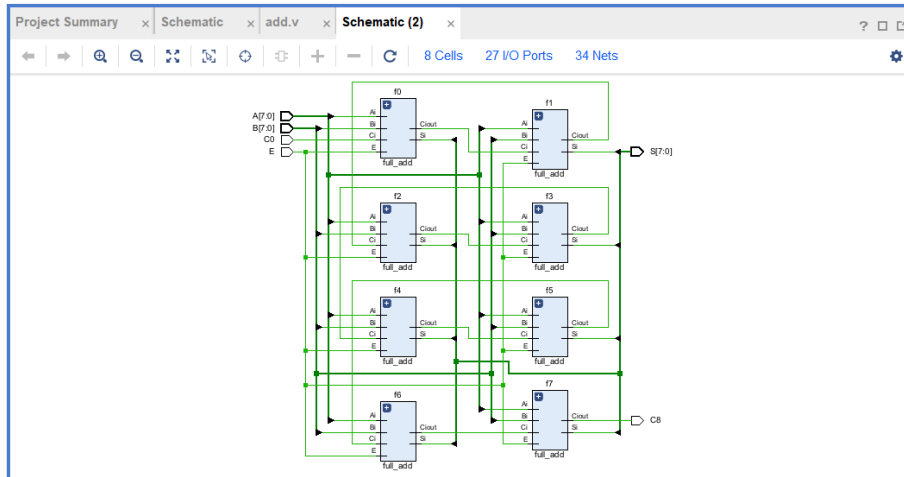

(d) ModelSim 源程序

```
module add_tb;

    reg [7:0] A, B;

    reg C0;

    reg E;

    wire [7:0] S;

    wire C8;

    add uut (

        .A(A),

        .B(B),

        .C0(C0),

        .E(E),

        .S(S),

        .C8(C8)

    );

    initial begin

        E = 1;

        A = 0;

        B = 0;
```

```

C0 = 0;


#10 A = 8'd50; B = 8'd70;
#10 A = 8'd255; B = 8'd1;
#10 E = 1'b0;
#10 A = 8'd150; B = 8'd100;
#10 A = 8'd200; B = 8'd55; C0 = 1'b1;
#10 A = 8'd0; B = 8'd0;
#10 A = 8'd128; B = 8'd128;
#10 A = 8'd127; B = 8'd1;
#10 A = 8'd255; B = 8'd255;

#30 A = 1'd0; B = 1'd0;

end
endmodule

```

(d) ModelSim 仿真结果

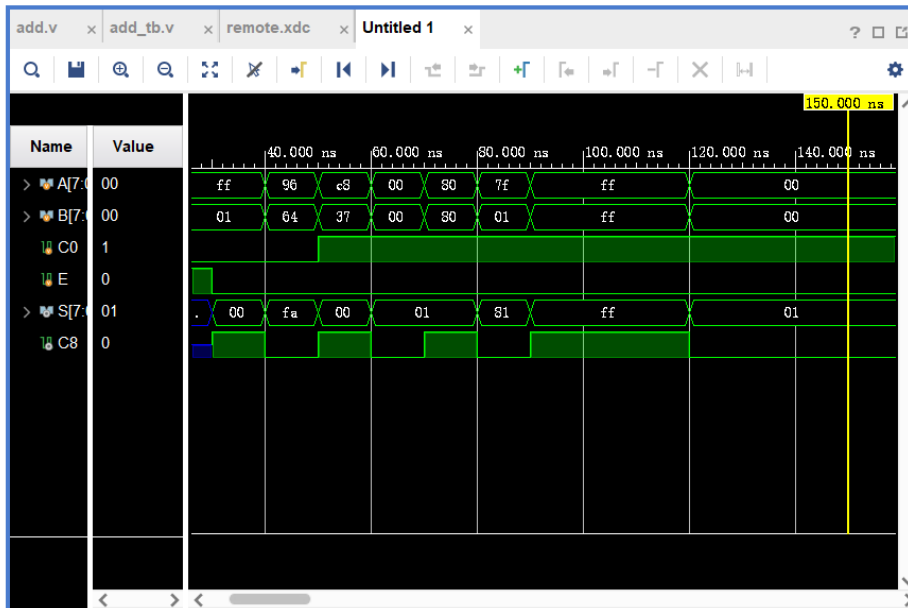

(e) 下载测试结

管脚配置

```

set_property -dict {PACKAGE_PIN B24 IOSTANDARD LVCMOS33} [get_ports {S[0]}]
set_property -dict {PACKAGE_PIN E21 IOSTANDARD LVCMOS33} [get_ports {S[1]}]
set_property -dict {PACKAGE_PIN A24 IOSTANDARD LVCMOS33} [get_ports {S[2]}]
set_property -dict {PACKAGE_PIN D23 IOSTANDARD LVCMOS33} [get_ports {S[3]}]
set_property -dict {PACKAGE_PIN C22 IOSTANDARD LVCMOS33} [get_ports {S[4]}]


```

```

set_property -dict {PACKAGE_PIN C21 IOSTANDARD LVCMOS33} [get_ports {S[5]}]
set_property -dict {PACKAGE_PIN E20 IOSTANDARD LVCMOS33} [get_ports {S[6]}]
set_property -dict {PACKAGE_PIN B22 IOSTANDARD LVCMOS33} [get_ports {S[7]}]
set_property -dict {PACKAGE_PIN C23 IOSTANDARD LVCMOS33} [get_ports {C8}]
set_property -dict {PACKAGE_PIN T3 IOSTANDARD LVCMOS33} [get_ports {A[0]}]
set_property -dict {PACKAGE_PIN J3 IOSTANDARD LVCMOS33} [get_ports {A[1]}]
set_property -dict {PACKAGE_PIN M2 IOSTANDARD LVCMOS33} [get_ports {A[2]}]
set_property -dict {PACKAGE_PIN P1 IOSTANDARD LVCMOS33} [get_ports {A[3]}]
set_property -dict {PACKAGE_PIN P4 IOSTANDARD LVCMOS33} [get_ports {A[4]}]
set_property -dict {PACKAGE_PIN L5 IOSTANDARD LVCMOS33} [get_ports {A[5]}]
set_property -dict {PACKAGE_PIN L3 IOSTANDARD LVCMOS33} [get_ports {A[6]}]
set_property -dict {PACKAGE_PIN N6 IOSTANDARD LVCMOS33} [get_ports {A[7]}]
set_property -dict {PACKAGE_PIN M6 IOSTANDARD LVCMOS33} [get_ports {B[0]}]
set_property -dict {PACKAGE_PIN N7 IOSTANDARD LVCMOS33} [get_ports {B[1]}]
set_property -dict {PACKAGE_PIN M7 IOSTANDARD LVCMOS33} [get_ports {B[2]}]
set_property -dict {PACKAGE_PIN L7 IOSTANDARD LVCMOS33} [get_ports {B[3]}]
set_property -dict {PACKAGE_PIN M5 IOSTANDARD LVCMOS33} [get_ports {B[4]}]
set_property -dict {PACKAGE_PIN K3 IOSTANDARD LVCMOS33} [get_ports {B[5]}]
set_property -dict {PACKAGE_PIN J1 IOSTANDARD LVCMOS33} [get_ports {B[6]}]
set_property -dict {PACKAGE_PIN L2 IOSTANDARD LVCMOS33} [get_ports {B[7]}]
set_property -dict {PACKAGE_PIN K2 IOSTANDARD LVCMOS33} [get_ports {E}]
set_property -dict {PACKAGE_PIN K1 IOSTANDARD LVCMOS33} [get_ports {C0}]

```

测试图

 

## 2. 扩展任务

(1)

源程序

```
module adder4(  
  
    input wire C0,  
  
    input wire [3:0] A,  
  
    input wire [3:0] B,  
  
    output wire C4,  
  
    output wire [3:0] S);  
  
    wire C1,C2,C3;  
  
    wire G0,G1,G2,G3;  
  
    wire P0,P1,P2,P3;  
  
    assign P0=A[0]|B[0];  
  
    assign P1=A[1]|B[1];  
  
    assign P2=A[2]|B[2];  
  
    assign P3=A[3]|B[3];  
  
    assign G0=A[0]&B[0];  
  
    assign G1=A[1]&B[1];  
  
    assign G2=A[2]&B[2];  
  
    assign G3=A[3]&B[3];  
  
    assign C1=G0|(C0&P0);  
  
    assign C2=G1|(C1&P1);  
  
    assign C3=G2|(C2&P2);  
  
    assign C4=G3|(C3&P3);
```

```
assign S[0]=A[0]^B[0]^C0;
```

```
assign S[1]=A[1]^B[1]^C1;
```

```
assign S[2]=A[2]^B[2]^C2;
```

```
assign S[3]=A[3]^B[3]^C3;
```

```
endmodule
```

```
module adder8(
```

```
    input wire C0,
```

```
    input wire [7:0] A,
```

```
    input wire [7:0] B,
```

```
    output wire [7:0] S,
```

```
    output wire C8);
```

```
    wire C4,C8;
```

```
    adder4 u0(
```

```
        .C0(C0),
```

```
        .A(A[3:0]),
```

```
        .B(B[3:0]),
```

```
        .S(S[3:0]),
```

```
        .C4(C4));
```

```
    adder4 u1(
```

```
        .C0(C4),
```

```
        .A(A[7:4]),
```


```
        .B(B[7:4]),
```

```
        .S(S[7:4]),
```

```
.C4(C8));
```

```
Endmodule
```

RTL 视图

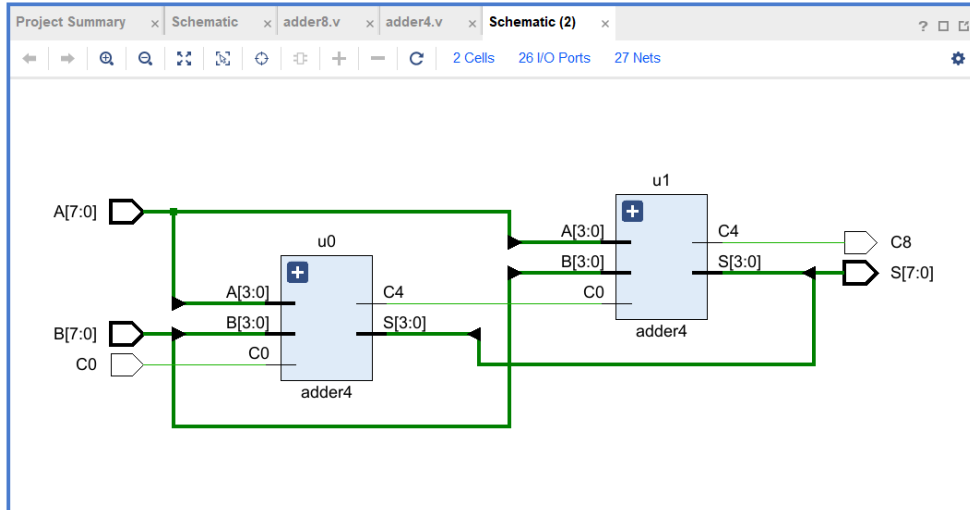

仿真源程序

```
module add_tb;
```

```
    reg [7:0] A, B;
```

```
    reg C0;
```

```
    reg E;
```

```
    wire [7:0] S;
```

```
    wire C8;
```

```
    add uut (
```

```
        .A(A),
```

```
        .B(B),
```

```
        .C0(C0),
```

```
        .E(E),
```

.S(S),

.C8(C8)

);

initial begin

E = 1;

A = 0;

B = 0;

C0 = 0;

#10 A = 8'd50; B = 8'd70;

#10 A = 8'd255; B = 8'd1;

#10 E = 1'b0;

#10 A = 8'd150; B = 8'd100;

#10 A = 8'd200; B = 8'd55;

#10 A = 8'd0; B = 8'd0; C0 = 1;

#10 A = 8'd128; B = 8'd128;

#10 A = 8'd127; B = 8'd1;

#10 A = 8'd255; B = 8'd255;


#10 A = 1'd0; B = 1'd0;

#10 \$stop;

end

endmodule

仿真截图

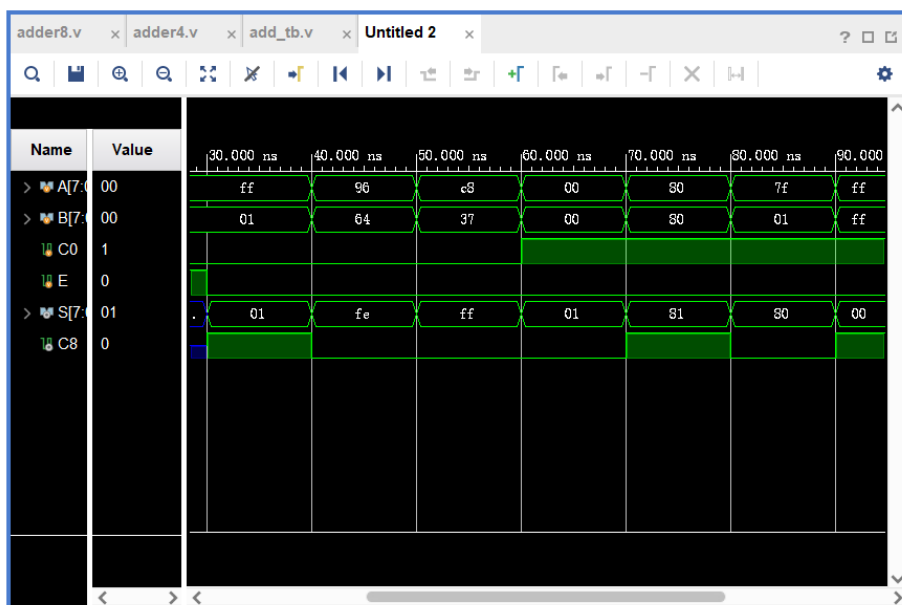

### 管脚配置

#LEDS

```
set_property -dict {PACKAGE_PIN B24 IOSTANDARD LVCMOS33} [get_ports {S[0]}]
```

```
set_property -dict {PACKAGE_PIN E21 IOSTANDARD LVCMOS33} [get_ports {S[1]}]
```

```
set_property -dict {PACKAGE_PIN A24 IOSTANDARD LVCMOS33} [get_ports {S[2]}]
```

```
set_property -dict {PACKAGE_PIN D23 IOSTANDARD LVCMOS33} [get_ports {S[3]}]
```

```
set_property -dict {PACKAGE_PIN C22 IOSTANDARD LVCMOS33} [get_ports {S[4]}]
```

```
set_property -dict {PACKAGE_PIN C21 IOSTANDARD LVCMOS33} [get_ports {S[5]}]
```

```
set_property -dict {PACKAGE_PIN E20 IOSTANDARD LVCMOS33} [get_ports {S[6]}]
```

```
set_property -dict {PACKAGE_PIN B22 IOSTANDARD LVCMOS33} [get_ports {S[7]}]
```

```
set_property -dict {PACKAGE_PIN C23 IOSTANDARD LVCMOS33} [get_ports {C8}]
```

#DIP\_SW

```
set_property -dict {PACKAGE_PIN T3 IOSTANDARD LVCMOS33} [get_ports {A[0]}]
```



```
set_property -dict {PACKAGE_PIN J3 IOSTANDARD LVCMOS33} [get_ports {A[1]]}

set_property -dict {PACKAGE_PIN M2 IOSTANDARD LVCMOS33} [get_ports {A[2]]}

set_property -dict {PACKAGE_PIN P1 IOSTANDARD LVCMOS33} [get_ports {A[3]]}

set_property -dict {PACKAGE_PIN P4 IOSTANDARD LVCMOS33} [get_ports {A[4]]}

set_property -dict {PACKAGE_PIN L5 IOSTANDARD LVCMOS33} [get_ports {A[5]]}

set_property -dict {PACKAGE_PIN L3 IOSTANDARD LVCMOS33} [get_ports {A[6]]}

set_property -dict {PACKAGE_PIN N6 IOSTANDARD LVCMOS33} [get_ports {A[7]]}

set_property -dict {PACKAGE_PIN M6 IOSTANDARD LVCMOS33} [get_ports {C0}]

set_property -dict {PACKAGE_PIN N7 IOSTANDARD LVCMOS33} [get_ports {B[0]]}

set_property -dict {PACKAGE_PIN M7 IOSTANDARD LVCMOS33} [get_ports {B[1]]}

set_property -dict {PACKAGE_PIN L7 IOSTANDARD LVCMOS33} [get_ports {B[2]]}

set_property -dict {PACKAGE_PIN M5 IOSTANDARD LVCMOS33} [get_ports {B[3]]}

set_property -dict {PACKAGE_PIN K3 IOSTANDARD LVCMOS33} [get_ports {B[4]]}


set_property -dict {PACKAGE_PIN J1 IOSTANDARD LVCMOS33} [get_ports {B[5]]}

set_property -dict {PACKAGE_PIN L2 IOSTANDARD LVCMOS33} [get_ports {B[6]]}

set_property -dict {PACKAGE_PIN K2 IOSTANDARD LVCMOS33} [get_ports {B[7]]}

#set_property -dict {PACKAGE_PIN K1 IOSTANDARD LVCMOS33} [get_ports {C0}]
```

测试

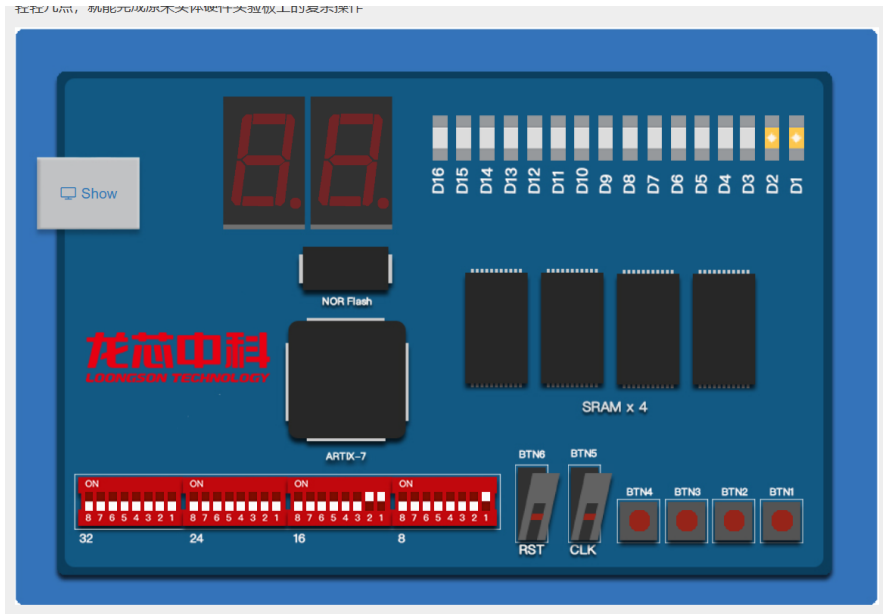

(2)

源程序

```
module full_add(

    input wire Ai,

    input wire Bi,

    input wire Ci,

    output reg Si,

    output reg Ciout

);

    wire S = Ci ^ Ai ^ Bi;

    wire C = Ai & Bi | (Ai ^ Bi) & Ci;

    always @ (*) begin

        Si = S;

        Ciout = C;

    end

endmodule
```

```
module add(

    input wire [7:0] A,

    input wire [7:0] B,

    input wire C0,

    output wire [7:0] S,

    output wire C8

);

    wire C1, C2, C3, C4, C5, C6, C7;

    full_add f0(

        .Ai(A[0]),

        .Bi(B[0]),

        .Ci(C0),

        .Si(S[0]),

        .Ciout(C1)

    );

    full_add f1(

        .Ai(A[1]),

        .Bi(B[1]),

        .Ci(C1),

        .Si(S[1]),

        .Ciout(C2)

    );

    full_add f2(
```

```
.Ai(A[2]),  
  
.Bi(B[2]),  
  
.Ci(C2),  
  
.Si(S[2]),  
  
.Ciout(C3)
```

```
);
```

```
full_add f3(  
  
.Ai(A[3]),  
  
.Bi(B[3]),  
  
.Ci(C3),  
  
.Si(S[3]),  
  
.Ciout(C4)
```

```
);
```

```
full_add f4(  
  
.Ai(A[4]),  
  
.Bi(B[4]),  
  
.Ci(C4),  
  
.Si(S[4]),  
  
.Ciout(C5)
```

```
)
```

```
full_add f5(  
  
.Ai(A[5]),  
  
.Bi(B[5]),
```

```
.Ci(C5),

.Si(S[5]),

.Ciout(C6)

);

full_add f6(

.Ai(A[6]),

.Bi(B[6]),

.Ci(C6),

.Si(S[6]),

.Ciout(C7)

);

full_add f7(

.Ai(A[7]),

.Bi(B[7]),

.Ci(C7),

.Si(S[7]),

.Ciout(C8)

);

endmodule

module full_sub(

    input wire A,

    input wire B,

    input wire Cin,
```

```
output reg D,  
  
output reg Co  
  
);  
  
always @ (*) begin  
  
    D = A ^ (B ^ Cin);  
  
    Co = ~A & (B ^ Cin) | Cin & B;  
  
end  
  
endmodule
```

```
module sub(  
  
    input wire [7:0] A,  
  
    input wire [7:0] B,  
  
    input wire C0,  
  
    output wire [7:0] D,  
  
    output wire B8  
  
);  
  
    wire B1, B2, B3, B4, B5, B6, B7;  
  
    full_sub s0(  
  
        .A(A[0]),  
  
        .B(B[0]),  
  
        .Cin(C0),  
  
        .D(D[0]),  
  
        .Co(B1)
```

);

full\_sub s1(

.A(A[1]),

.B(B[1]),

.Cin(B1),

.D(D[1]),

.Co(B2)

);

full\_sub s2(

.A(A[2]),

.B(B[2]),

.Cin(B2),

.D(D[2]),

.Co(B3)

);

full\_sub s3(

.A(A[3]),

.B(B[3]),

.Cin(B3),

.D(D[3]),

.Co(B4)

);

full\_sub s4(

```
.A(A[4]),  
  
.B(B[4]),  
  
.Cin(B4),  
  
.D(D[4]),  
  
.Co(B5)
```

```
);
```

```
full_sub s5(  
  
    .A(A[5]),  
  
    .B(B[5]),  
  
    .Cin(B5),  
  
    .D(D[5]),  
  
    .Co(B6)
```

```
);
```

```
full_sub s6(  
  
    .A(A[6]),  
  
    .B(B[6]),  
  
    .Cin(B6),  
  
    .D(D[6]),  
  
    .Co(B7)
```

```
);
```

```
full_sub s7(  
  
    .A(A[7]),  
  
    .B(B[7]),
```



```
.Cin(B7),

.D(D[7]),

.Co(B8)

);

endmodule

module addAndSub(

    input wire [7:0] A,

    input wire [7:0] B,

    input wire E, // 控制信号, 1 表示加法, 0 表示减法

    input wire C0,

    output wire [7:0] Result,

    output wire C

);

    wire [7:0] sum;

    wire [7:0] diff;

    wire sum_carry;

    wire borrow;

    add adder(

        .A(A),

        .B(B),

        .C0(C0),

        .S(sum),

        .C8(sum_carry)
```

);

sub subtractor(

.A(A),

.B(B),

.C0(C0),

.D(diff),

.B8(borrow)


);

assign Result = (E) ? sum : diff;

assign C = (E) ? sum\_carry : borrow;

endmodule

## RTL 视图

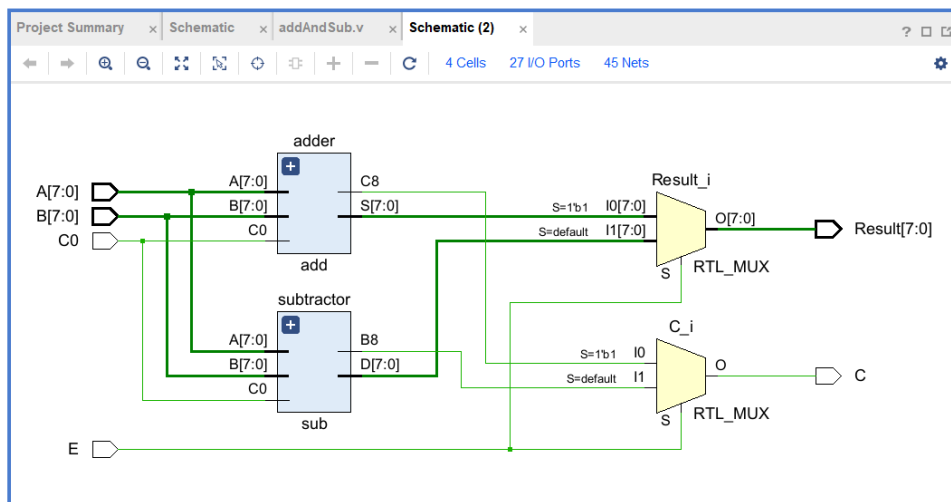

## 仿真程序

module addAndSub\_tb;

reg [7:0] A, B;

reg C0;

```
reg E;

wire [7:0] Result;

wire C;

addAndSub uut (

    .A(A),

    .B(B),

    .C0(C0),

    .E(E),

    .Result(Result),

    .C(C)

);

initial begin

    E = 1;

    A = 0;

    B = 0;

    C0 = 1;

    #10 A = 8'd50; B = 8'd70;

    #10 A = 8'd255; B = 8'd1;

    #10 E = 1'b0;

    #10 A = 8'd150; B = 8'd100;

    #10 A = 8'd200; B = 8'd55;

    #10 A = 8'd0; B = 8'd0; C0 = 0;

    #10 A = 8'd128; B = 8'd128; C0 = 1;
```

```
#10 A = 8'd127; B = 8'd1;
```


```
#10 A = 8'd255; B = 8'd255;
```

```
#10 A = 1'd0; B = 1'd0;
```

```
end
```

```
endmodule
```

## 仿真截图

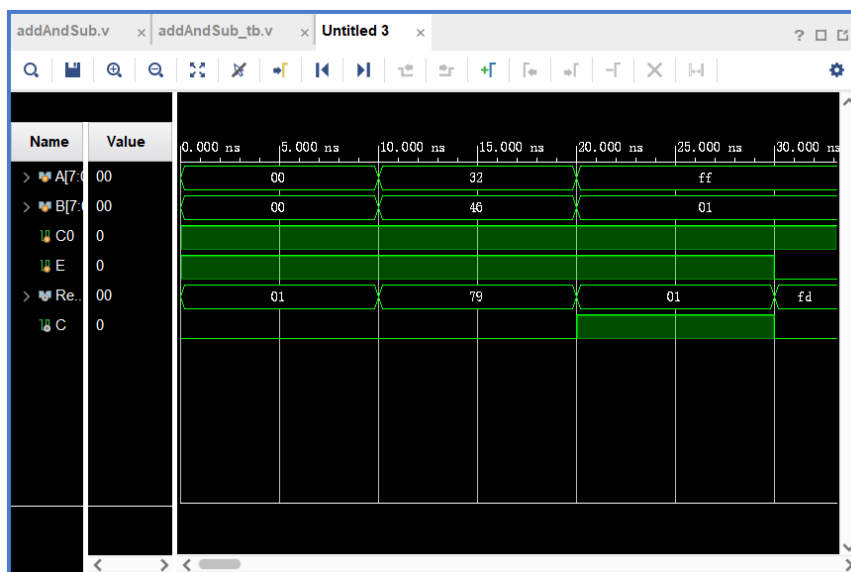

## 管脚配置

```
#LEDS
```

```
set_property -dict {PACKAGE_PIN B24 IOSTANDARD LVCMOS33} [get_ports {Result[0]}]
```

```
set_property -dict {PACKAGE_PIN E21 IOSTANDARD LVCMOS33} [get_ports {Result[1]}]
```

```
set_property -dict {PACKAGE_PIN A24 IOSTANDARD LVCMOS33} [get_ports {Result[2]}]
```

```
set_property -dict {PACKAGE_PIN D23 IOSTANDARD LVCMOS33} [get_ports {Result[3]}]
```

```
set_property -dict {PACKAGE_PIN C22 IOSTANDARD LVCMOS33} [get_ports {Result[4]}]
```

```
set_property -dict {PACKAGE_PIN C21 IOSTANDARD LVCMOS33} [get_ports {Result[5]}]
```

```
set_property -dict {PACKAGE_PIN E20 IOSTANDARD LVCMOS33} [get_ports {Result[6]}]
```

set\_property -dict {PACKAGE\_PIN B22 IOSTANDARD LVCMOS33} [get\_ports {Result[7]}]

set\_property -dict {PACKAGE\_PIN C23 IOSTANDARD LVCMOS33} [get\_ports {C}]

#DIP\_SW

set\_property -dict {PACKAGE\_PIN T3 IOSTANDARD LVCMOS33} [get\_ports {A[0]}]

set\_property -dict {PACKAGE\_PIN J3 IOSTANDARD LVCMOS33} [get\_ports {A[1]}]

set\_property -dict {PACKAGE\_PIN M2 IOSTANDARD LVCMOS33} [get\_ports {A[2]}]

set\_property -dict {PACKAGE\_PIN P1 IOSTANDARD LVCMOS33} [get\_ports {A[3]}]

set\_property -dict {PACKAGE\_PIN P4 IOSTANDARD LVCMOS33} [get\_ports {A[4]}]

set\_property -dict {PACKAGE\_PIN L5 IOSTANDARD LVCMOS33} [get\_ports {A[5]}]

set\_property -dict {PACKAGE\_PIN L3 IOSTANDARD LVCMOS33} [get\_ports {A[6]}]

set\_property -dict {PACKAGE\_PIN N6 IOSTANDARD LVCMOS33} [get\_ports {A[7]}]

set\_property -dict {PACKAGE\_PIN M6 IOSTANDARD LVCMOS33} [get\_ports {E}]

set\_property -dict {PACKAGE\_PIN N7 IOSTANDARD LVCMOS33} [get\_ports {B[0]}]

set\_property -dict {PACKAGE\_PIN M7 IOSTANDARD LVCMOS33} [get\_ports {B[1]}]

set\_property -dict {PACKAGE\_PIN L7 IOSTANDARD LVCMOS33} [get\_ports {B[2]}]

set\_property -dict {PACKAGE\_PIN M5 IOSTANDARD LVCMOS33} [get\_ports {B[3]}]

set\_property -dict {PACKAGE\_PIN K3 IOSTANDARD LVCMOS33} [get\_ports {B[4]}]


set\_property -dict {PACKAGE\_PIN J1 IOSTANDARD LVCMOS33} [get\_ports {B[5]}]

set\_property -dict {PACKAGE\_PIN L2 IOSTANDARD LVCMOS33} [get\_ports {B[6]}]

set\_property -dict {PACKAGE\_PIN K2 IOSTANDARD LVCMOS33} [get\_ports {B[7]}]

set\_property -dict {PACKAGE\_PIN K1 IOSTANDARD LVCMOS33} [get\_ports {C0}]

测试

 

## 五、实验过程中出现的故障现象、原因分析及解决的办法

加法器最高位进位设置有误，导致溢出出现错误结果，设置最高位进位标志，处理溢出情况。